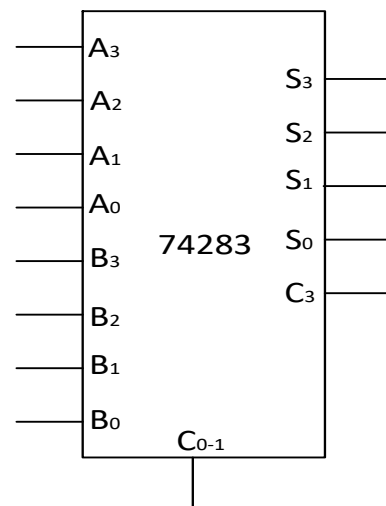


Name: _____ Student number: _____ SCORE: _____

Homework 3

- Show how the following expressions can be implemented as stated using only NAND gates:
 (a) $X = ABC$ (b) $Y = \overline{AB} + \overline{CD}$
- A 74HC147 encoder has LOW levels on pins 2, 5, and 12. What BCD code appears on the outputs if all the other inputs are HIGH?
- Show the logic required to convert a 10-bit binary number to Gray code and use that logic to convert the following binary numbers to Gray code:
 (a) 1010111100
 (b) 1111000011
- Please convert the 2421BCD codes to 5421BCD codes using the 74283 adder. Give analysis procedure and draw a conversion circuit on the adder directly.

2421BCD 码				5421BCD 码			
D	C	B	A	D	C	B	A
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
1	0	1	1	1	0	0	0
1	1	0	0	1	0	0	1
1	1	0	1	1	0	1	0
1	1	1	0	1	0	1	1
1	1	1	1	1	1	0	0



- Implement the logic function

$$F = A\overline{B}D + \overline{A}B\overline{C}D + BC + \overline{B}C\overline{D}$$

- (1) Use 74LS138s and NAND gates
- (2) Use 74HC151 and other logic gates necessary